

22583 Special Topics in Computer Engineering (2) Advanced Digital Systems Design and Verification

Lab 2: RTL Model of Two-Stage RISC-V Processor

March 13, 2024

1 Objectives

For the second lab assignment, you will write an RTL model of a two-stage pipelined RISC-V-v2 (a subset of the RISC-V instruction set) processor.

2 Tools

Use one of the following Verilog simulators (or any one of your choice):

- Intel® Quartus®
- www.edaplayground.com
- Download Verilog from: <http://bleyer.org/icarus/>

3 Design Activity

The two-stage pipeline should perform instruction fetch in the first stage, while the second pipeline stage should do everything else including data memory access. If you need to refresh your memory about pipelining and the RISC-V instruction set, we recommend Computer Organization and Design: The Hardware/Software Interface, by Patterson and Hennessey.

Make sure to separate out datapath and memory components from control circuitry. The system diagram in Figure 1 can be used as an initial template for your two-stage RISC-V-v2 processor implementation, but please treat it as a suggestion. Your objective in this lab is to implement the RISC-V-v2 ISA, not to implement the system diagram so feel free to add new control signals, merge modules, or make any other modifications to the system. You will need to turn in a diagram of your datapath anyway, so it is highly recommended that you draw your datapath from the beginning in a program such as Visio, and keep it updated as you design. This reference will be very useful to speed up debugging.

For this lab assignment, you will only be implementing a subset of the RISC-V specification. Figure 2 shows the instructions that you must support.

4 Design Flow

Strictly follow the following order:

1. Write the Verilog code for the circuits described above.
2. Write Verilog testbenches to test your modules.
3. Perform Functional Simulation (Run Simulation → Run Behavioral Simulation) and take snapshots of the results.

5 Deliverables

You will need to submit to E-learning (as a .zip file) including the following:

- The Verilog code: Your design should be modular.
- Verilog testbenches: test each module separately.
- Run logs: the run result for each test case (text and waveforms)

31	27	26	22	21	17	16	15	14	12	11	10	9	8	7	6	0	
jump target																opcode	J-type
rd	LUI-immediate															opcode	LUI-type
rd	rs1	imm[11:7]				imm[6:0]				funct3				opcode	I-type		
imm[11:7]	rs1	rs2				imm[6:0]				funct3				opcode	B-type		
rd	rs1	rs2				funct10								opcode	R-type		
rd	rs1	rs2				rs3				funct5				opcode	R4-type		

Control Transfer Instructions

imm25																1100111	J imm25
imm25																1101111	JAL imm25
imm12hi	rs1	rs2				imm12lo				000				1100011	BEQ rs1,rs2,imm12		
imm12hi	rs1	rs2				imm12lo				001				1100011	BNE rs1,rs2,imm12		
imm12hi	rs1	rs2				imm12lo				100				1100011	BLT rs1,rs2,imm12		
imm12hi	rs1	rs2				imm12lo				101				1100011	BGE rs1,rs2,imm12		
imm12hi	rs1	rs2				imm12lo				110				1100011	BLTU rs1,rs2,imm12		
imm12hi	rs1	rs2				imm12lo				111				1100011	BGEU rs1,rs2,imm12		
rd	rs1	imm12								000				1101011	JALR.C rd,rs1,imm12		
rd	rs1	imm12								001				1101011	JALR.R rd,rs1,imm12		
rd	rs1	imm12								010				1101011	JALR.J rd,rs1,imm12		

Memory Instructions

rd	rs1	imm12								010				0000011	LW rd,rs1,imm12
imm12hi	rs1	rs2				imm12lo				010				0100011	SW rs1,rs2,imm12

Integer Compute Instructions

rd	rs1	imm12								000				0010011	ADDI rd,rs1,imm12		
rd	rs1	000000				shamt				001				0010011	SLLI rd,rs1,shamt		
rd	rs1	imm12								010				0010011	SLTI rd,rs1,imm12		
rd	rs1	imm12								011				0010011	SLTIU rd,rs1,imm12		
rd	rs1	imm12								100				0010011	XORI rd,rs1,imm12		
rd	rs1	000000				shamt				101				0010011	SRLI rd,rs1,shamt		
rd	rs1	imm12								110				0010011	ORI rd,rs1,imm12		
rd	rs1	imm12								111				0010011	ANDI rd,rs1,imm12		
rd	rs1	rs2	0000000								000				0110011	ADD rd,rs1,rs2	
rd	rs1	rs2	1000000								000				0110011	SUB rd,rs1,rs2	
rd	rs1	rs2	0000000								001				0110011	SLL rd,rs1,rs2	
rd	rs1	rs2	0000000								010				0110011	SLT rd,rs1,rs2	
rd	rs1	rs2	0000000								011				0110011	SLTU rd,rs1,rs2	
rd	rs1	rs2	0000000								100				0110011	XOR rd,rs1,rs2	
rd	rs1	rs2	0000000								101				0110011	SRL rd,rs1,rs2	
rd	rs1	rs2	0000000								110				0110011	OR rd,rs1,rs2	
rd	rs1	rs2	0000000								111				0110011	AND rd,rs1,rs2	
rd	imm20															0110111	LUI rd,imm20

Figure 2: Instruction listing for RISC-V